

# Mathématiques discrètes et applications

## Discrete Mathematics and Applications

Problem Session 2

Peterson Yuhala

Instituts d'informatique et de mathématiques  
Université de Neuchâtel

Automne 2025 / Fall 2025



# Contact information

Peterson Yuhala

Office B119

[peterson.yuhala@unine.ch](mailto:peterson.yuhala@unine.ch)

## Exercise 1: 2-1 multiplexer

$S$	$I_1$	$I_2$	$M$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$M(S, I_1, I_2)_{DNF} = \bar{S}\bar{I}_1I_2 + \bar{S}I_1I_2 + SI_1\bar{I}_2 + SI_1I_2$$

Note: some documents suggest the DNF form does not necessarily have to contain all the boolean variables. However, the expression in **full DNF form** has all the input variables appearing exactly once.


## Exercise 1: Circuit for 2-1 multiplexer

Simplification of M:

$$\begin{aligned}M(S, I_1, I_2) &= \bar{S}\bar{I}_1I_2 + \bar{S}I_1I_2 + S\bar{I}_1\bar{I}_2 + SI_1\bar{I}_2 \\&\equiv \bar{S}I_2 \cdot (\bar{I}_1 + I_1) + S\bar{I}_1 \cdot (\bar{I}_2 + I_2) \\&\equiv S\bar{I}_1 + \bar{S}I_2\end{aligned}$$

**Distributive law**

**Negation law**

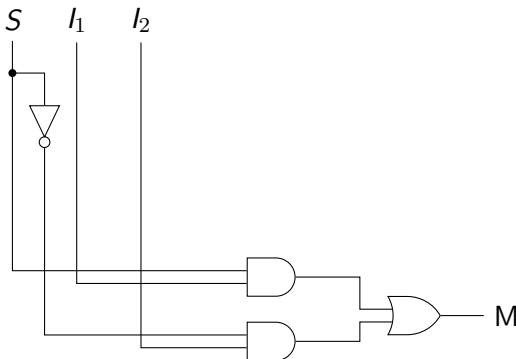

## Exercise 1: 2-1 multiplexer with NAND gates only


$$M(S, I_1, I_2) = SI_1 + \bar{S}I_2$$

$$\equiv \overline{\overline{SI_1 + \bar{S}I_2}}$$

**Double negative law**

$$\equiv (\overline{SI_1} \cdot \overline{\bar{S}I_2})$$

**De Morgan's law**

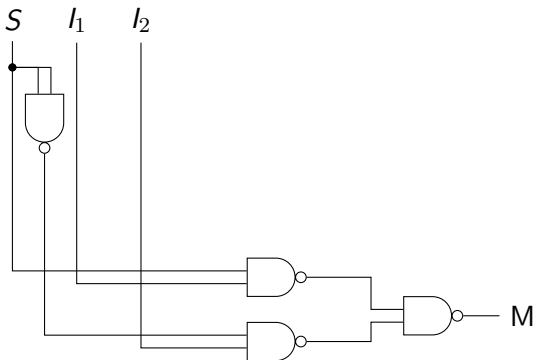

## Exercise 1: $M$ in conjunctive normal form (CNF)

Hint: To obtain the (full) CNF, we look at the rows of the truth table where  $\bar{M} = 1$ , i.e., where  $M = 0$ .


We find the DNF for  $\bar{M}$  and then use the property  $\bar{\bar{M}} \equiv M$  to obtain  $M$  in conjunctive normal form.

$$\begin{aligned}\bar{M}(S, I_1, I_2) &= \bar{S}\bar{I}_1\bar{I}_2 + \bar{S}I_1\bar{I}_2 + S\bar{I}_1\bar{I}_2 + S\bar{I}_1I_2 \\ \rightarrow M(S, I_1, I_2) &= \overline{\bar{S}\bar{I}_1\bar{I}_2 + \bar{S}I_1\bar{I}_2 + S\bar{I}_1\bar{I}_2 + S\bar{I}_1I_2} \\ &\equiv (\overline{\bar{S}\bar{I}_1\bar{I}_2}) \cdot (\overline{\bar{S}I_1\bar{I}_2}) \cdot (\overline{S\bar{I}_1\bar{I}_2}) \cdot (\overline{S\bar{I}_1I_2}) \\ &\equiv (S + I_1 + I_2) \cdot (S + \bar{I}_1 + I_2) \cdot (\bar{S} + I_1 + I_2) \cdot (\bar{S} + I_1 + \bar{I}_2)\end{aligned}$$

$$M(S, I_1, I_2)_{CNF} = (S + I_1 + I_2) \cdot (S + \bar{I}_1 + I_2) \cdot (\bar{S} + I_1 + I_2) \cdot (\bar{S} + I_1 + \bar{I}_2)$$
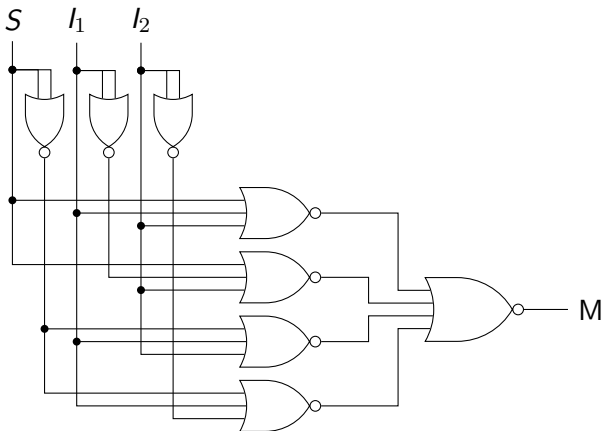
## Exercise 1: M with NOR gates only

$$\begin{aligned} M(S, I_1, I_2) &= \overline{\overline{(S + I_1 + I_2)} \cdot \overline{(S + \bar{I}_1 + I_2)} \cdot \overline{(\bar{S} + I_1 + I_2)} \cdot \overline{(\bar{S} + I_1 + \bar{I}_2)}} \\ &\equiv \overline{\overline{(S + I_1 + I_2)} + \overline{(S + \bar{I}_1 + I_2)} + \overline{(\bar{S} + I_1 + I_2)} + \overline{(\bar{S} + I_1 + \bar{I}_2)}} \end{aligned}$$



## Ex-2: useful terms

- An **implicant** (I) is a conjunction of literals (in sum-of-product form) or disjunction of literals (in product-of-sums form) in the expression of a boolean function  $F$ . That is,  $I \text{ true} \rightarrow F \text{ true}$ . Two or more implicants can be combined to obtain implicants with fewer literals.
- A **prime implicant** (PI) is one which cannot be combined further to obtain another implicant.
- An **essential prime implicant** (EPI) is a prime implicant which covers a minterm alone. That is, no other PI covers that minterm; an EPI **MUST** be part of the minimized form of a boolean function.



## Ex-2a: $F(x, y)$ in DNF

$x_1$	$x_2$	$y_1$	$y_2$	$F$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$\begin{aligned} F(x_1, x_2, y_1, y_2)_{DNF} = & \bar{x}_1 \bar{x}_2 \bar{y}_1 \bar{y}_2 + x_1 \bar{x}_2 \bar{y}_1 \bar{y}_2 + x_1 \bar{x}_2 \bar{y}_1 y_2 \\ & + x_1 x_2 \bar{y}_1 \bar{y}_2 + x_1 x_2 \bar{y}_1 y_2 + x_1 x_2 y_1 \bar{y}_2 \end{aligned}$$

## Ex-2b: Minimization of F with Quine-McCluskey

Table: Stage 1

Num. of 1 <sub>s</sub>	Minterm	Bit String
1	$m_4$	0100✓
	$m_8$	1000✓
2	$m_9$	1001✓
	$m_{12}$	1100✓
3	$m_{13}$	1101✓
	$m_{14}$	1110✓

Table: Stage 2

Size 2 Implicants	Bits
$m(4, 12)$	-100*
$m(8, 9)$	100-✓
$m(8, 12)$	1-00✓
$m(9, 13)$	1-01✓
$m(12, 13)$	110-✓
$m(12, 14)$	11-0*

## Ex-2b: Minimization of F with Quine-McCluskey

Stage 3:	Size 4 Implicants	Bits
	$m(8, 9, 12, 13)$	1-0-*
	$m(8, 12, 9, 13)$	1-0-*


NB: The goal here is to cover all the minterms with the **smallest subset of prime implicants**. All essential prime implicants must be part of the minimized expression.

Prime Implicants	Minterms	4	8	9	12	13	14
$x_2\bar{y}_1\bar{y}_2$	4,12	(X)			X		
$x_1x_2\bar{y}_2$	12,14				X		(X)
$x_1\bar{y}_1$	8,9,12,13		(X)	(X)	X	(X)	

$$F(x, y)_{min} = x_2\bar{y}_1\bar{y}_2 + x_1x_2\bar{y}_2 + x_1\bar{y}_1$$
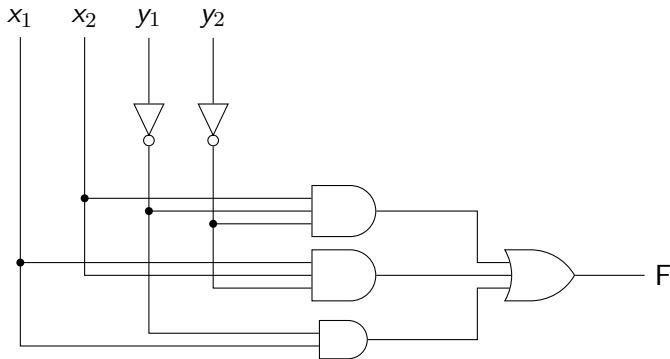
## Ex-2b: Circuit of $F_{min}$ with NOT, AND, and OR gates

$$F(x, y)_{min} = x_2 \bar{y}_1 \bar{y}_2 + x_1 x_2 \bar{y}_2 + x_1 \bar{y}_1$$




## Ex-2b: Circuit of $F_{min}$ with NAND gates only

$$\begin{aligned} F(x, y) &= \overline{\overline{(x_2 \bar{y}_1 \bar{y}_2)} + (x_1 x_2 \bar{y}_2) + (x_1 \bar{y}_1)} \\ &\equiv \overline{\overline{(x_2 \bar{y}_1 \bar{y}_2)} \cdot \overline{(x_1 x_2 \bar{y}_2)} \cdot \overline{(x_1 \bar{y}_1)}} \end{aligned}$$

**Double negative law**

**De Morgan's law**

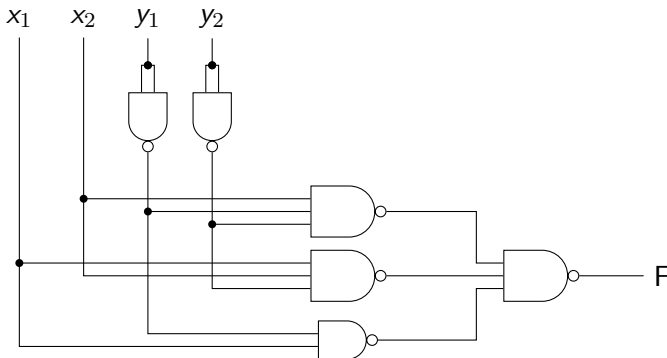

# End

For more exercises and notes, see Rosen 7th Edition Chap. 12.